
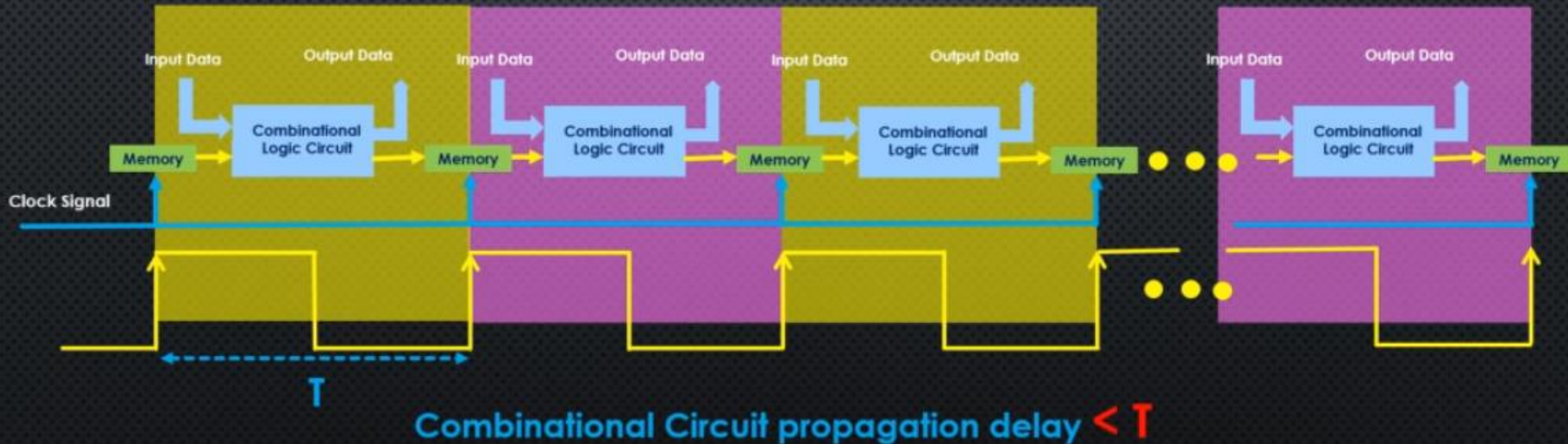
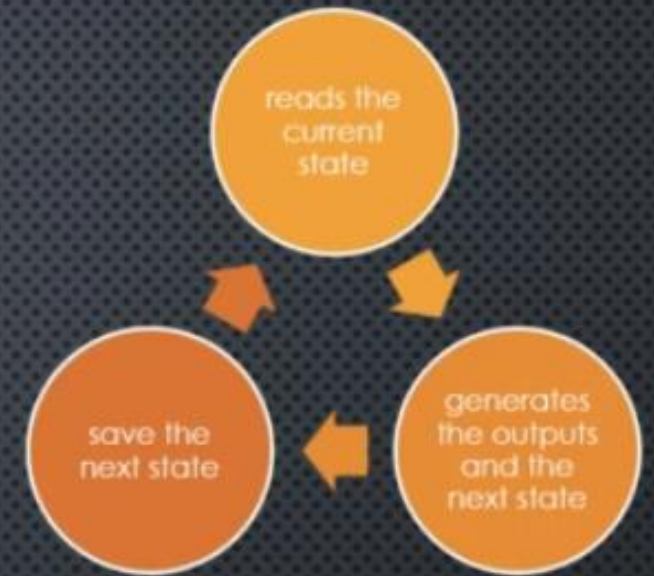



SINGLE CYCLE DESIGN FLOW

Lecture-9

SEQUENTIAL CIRCUIT MODEL

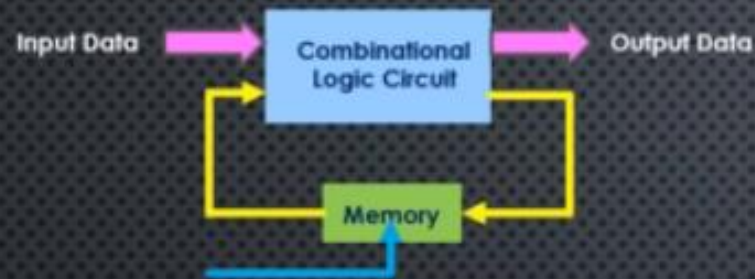

SEQUENTIAL CIRCUIT DESIGN IDEA

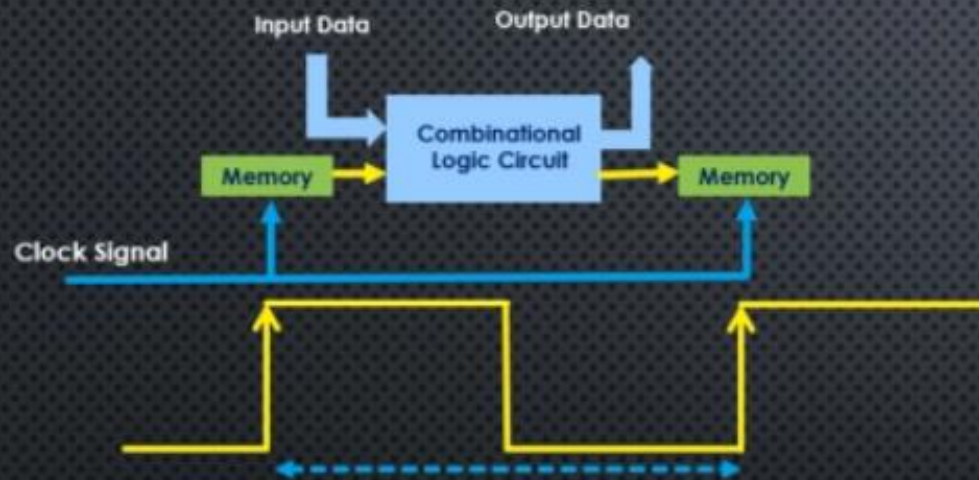

```
void func (arguments) {  
    define registers;  
  
    read register values  
    perform tasks  
    modify register values  
}
```



We use static variable definition in C/C++ to declare registers in HLS.

SINGLE-CYCLE DESIGN

The key idea in this section is developing a one-clock-cycle design


The single-cycle design approach can provide a high-performance hardware comparable with the HDL descriptions.

PARALLEL TO SERIAL


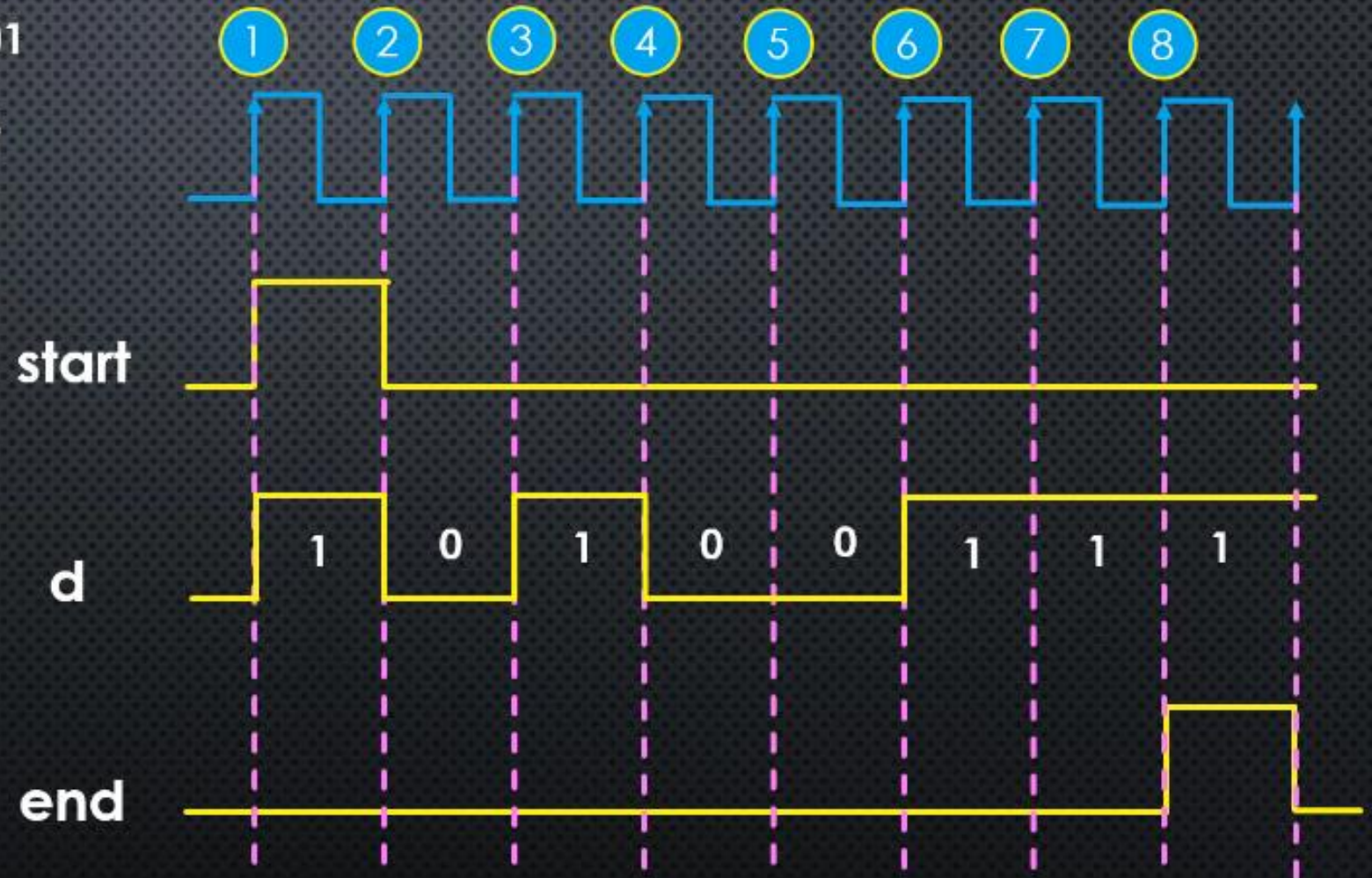
 


PARALLEL TO SERIAL


Data : 11100101

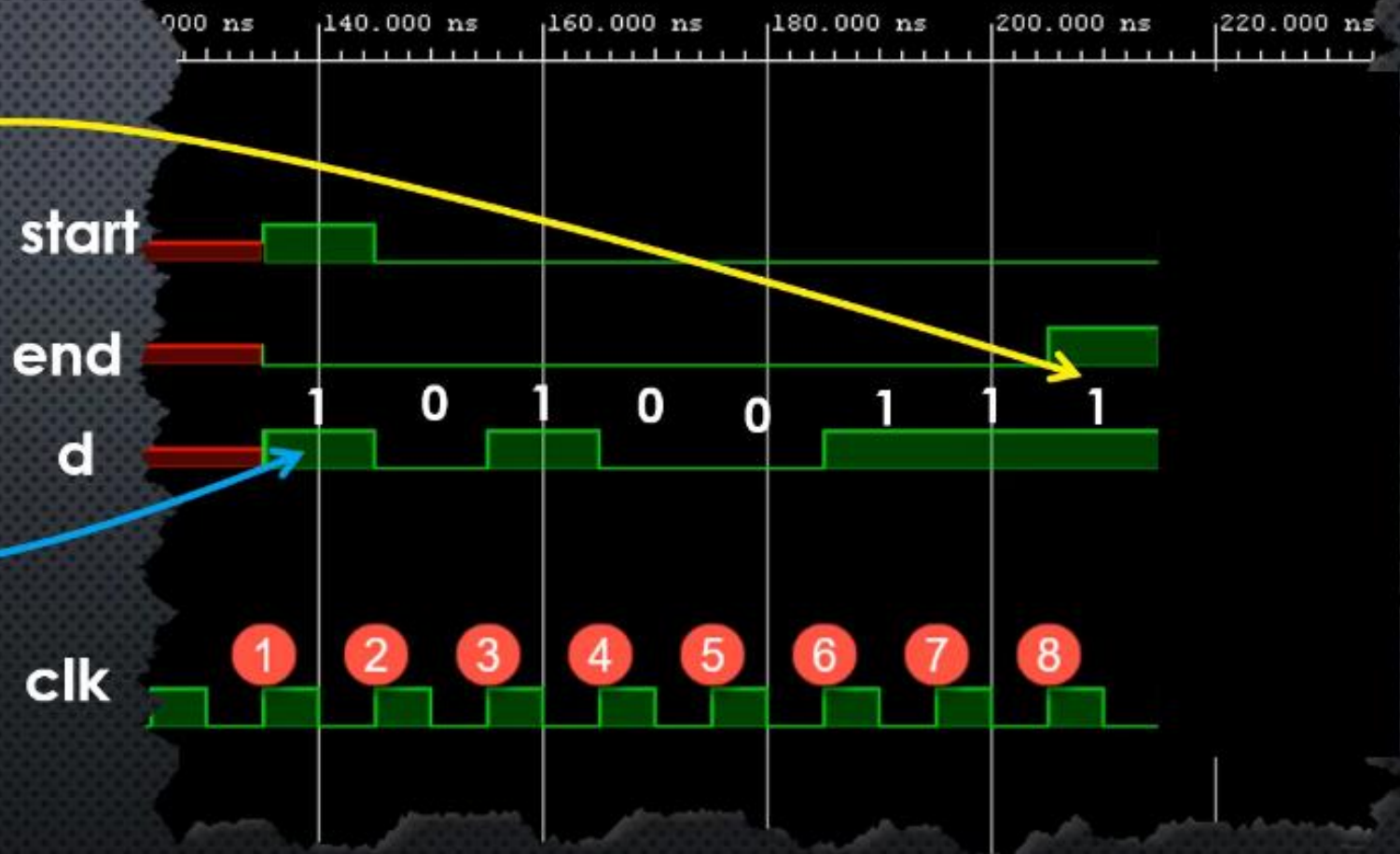


DESIGN

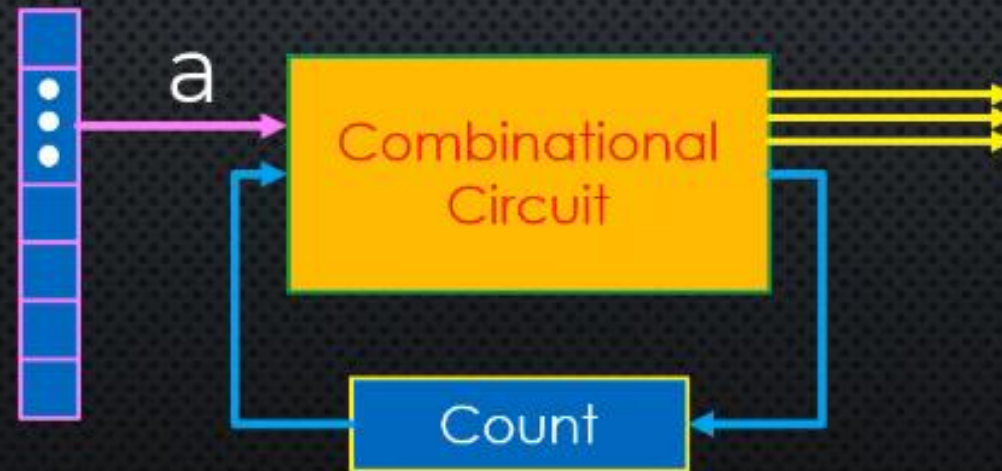  


SINGLE-CYCLE DESIGN

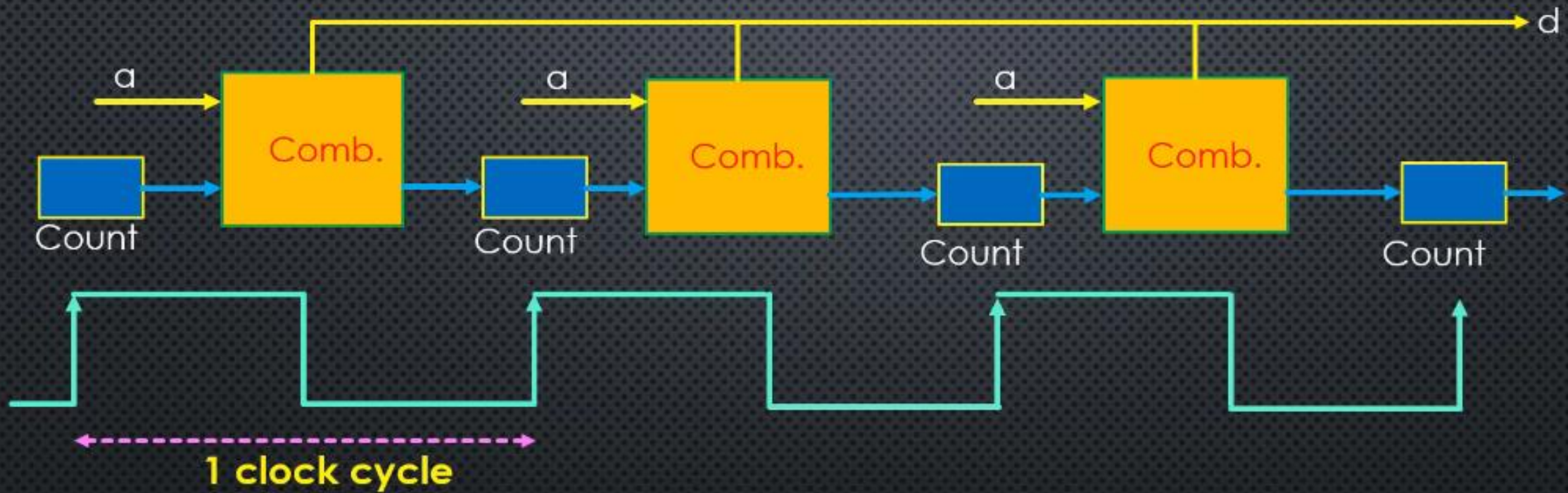

SINGLE-CYCLE DESIGN

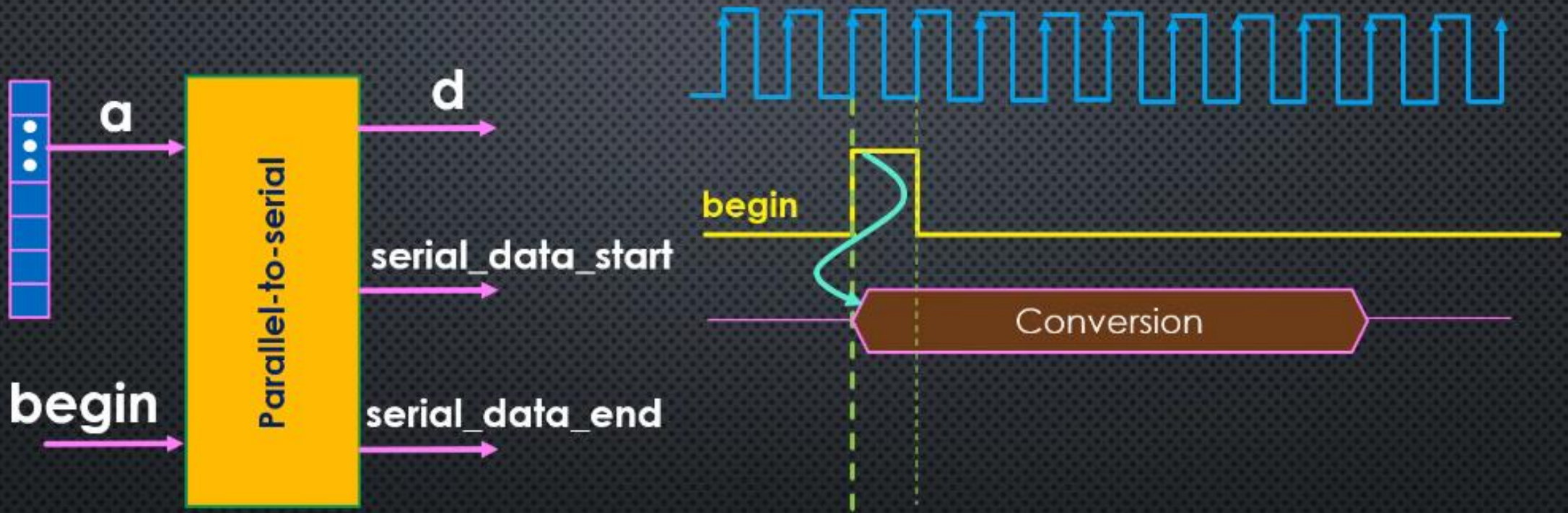

CODE FLOWCHART


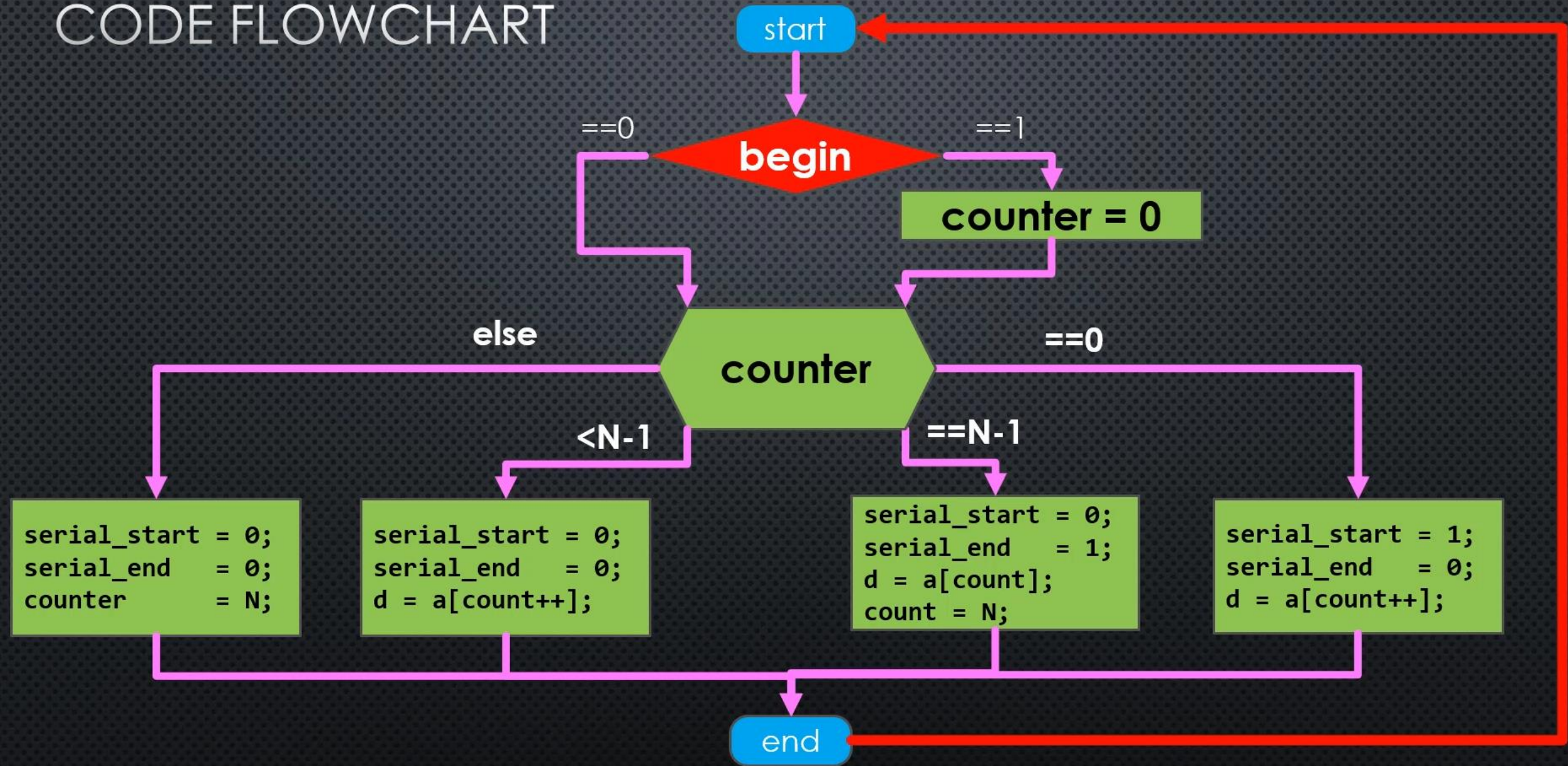


PARALLEL TO SERIAL CODE

```
void parallel2serial(  
    ap_uint<N> a,  
    bool      &d,  
    bool      &start_serial_data,  
    bool      &end_serial_data,  
    bool      begin) {  
  
    static int count = N;  
    if (begin == 1) {  
        count = 0;  
    }  
    if (count == 0) {  
        start_serial_data = 1;  
        end_serial_data   = 0;  
        d = a[count++];  
    }
```

```
    } else if (count == N-1) {  
        start_serial_data = 0;  
        end_serial_data   = 1;  
        d = a[count];  
        count = N;  
    } else if (count < N-1) {  
        start_serial_data = 0;  
        end_serial_data   = 0;  
        d = a[count++];  
    } else {  
        start_serial_data = 0;  
        end_serial_data   = 0;  
    }  
}
```

SERIAL TO PARALLEL

  


```
void serial2parallel(bool start_serial_data, bool &end_conversion, bool d, ap_uint<N> &a) {  
  
    static ap_uint<N> state_reg = 0;  
    static ap_uint<N> a_reg_out = 0;  
    static unsigned int counter = N;  
  
    unsigned int next_counter;  
    ap_uint<N> next_state = state_reg;  
  
    next_counter = counter;  
  
    if (start_serial_data == 1) {  
        next_counter = 0;  
    }  
}
```

```

if (next_counter < N-1) {
    next_state = (next_state >> 1) | (d, (ap_uint<N-1>)0);
    next_counter++;
    end_conversion = 0;
} else if (next_counter == N-1) {
    next_state = (next_state >> 1) | (d, (ap_uint<N-1>)0);
    next_counter++;
    a_reg_out = next_state;
    end_conversion = 1;
} else {
    end_conversion = 0;
}

```

```

counter    = next_counter;
state_reg  = next_state;
a          = a_reg_out;

```

```

}

```


start_serial_data

d

Combinational
Circuit


end_conversion

state_reg




counter

a_reg_out



a

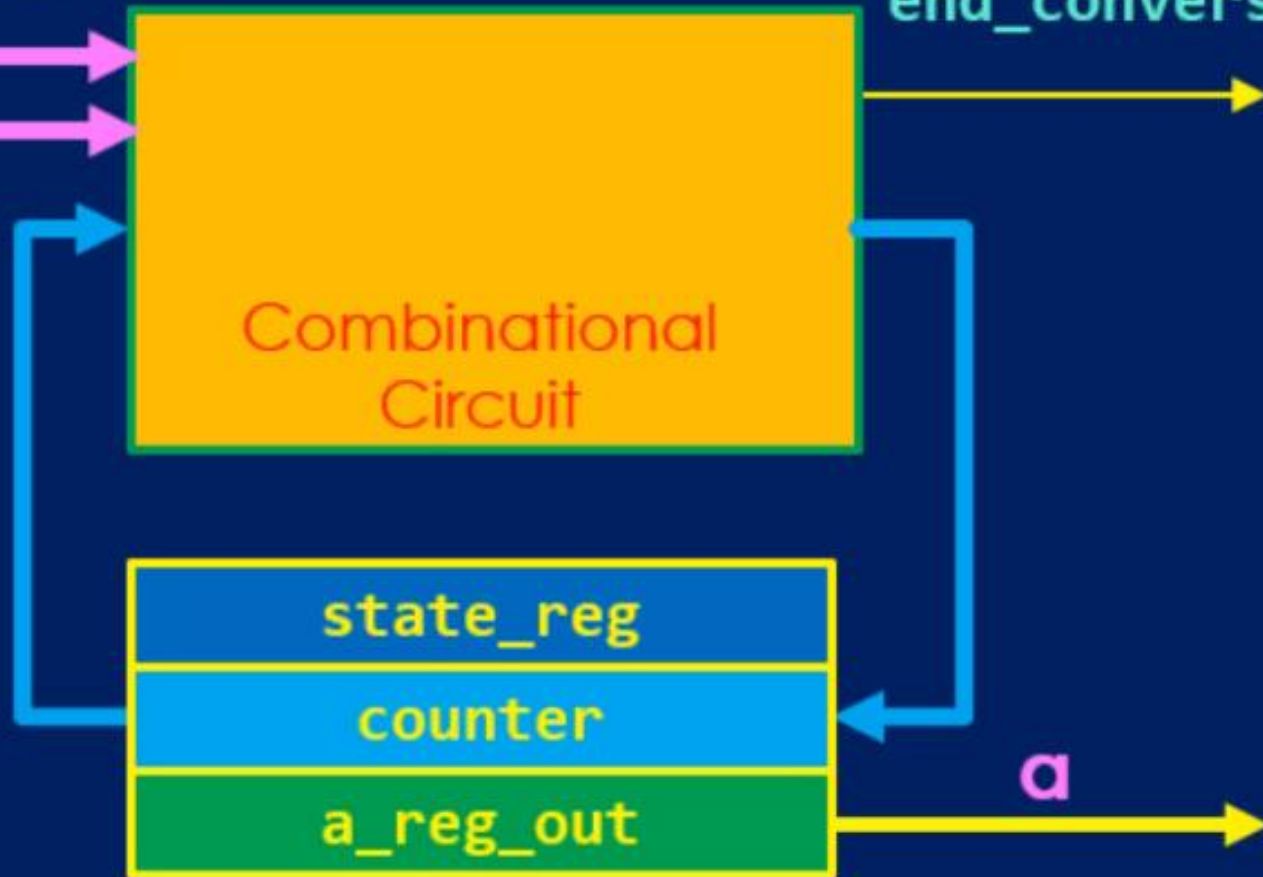

COMBINATIONAL CIRCUIT OUTPUT

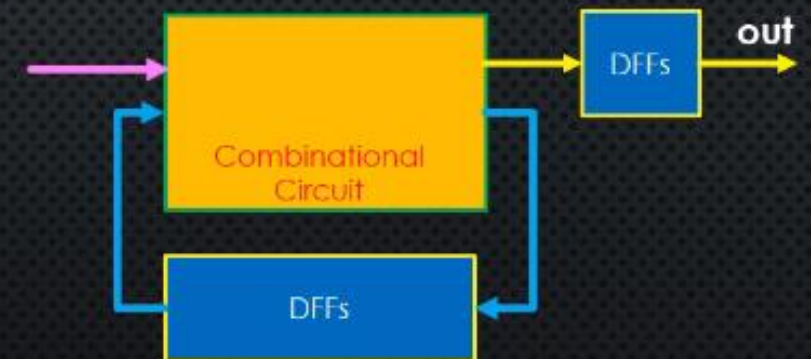 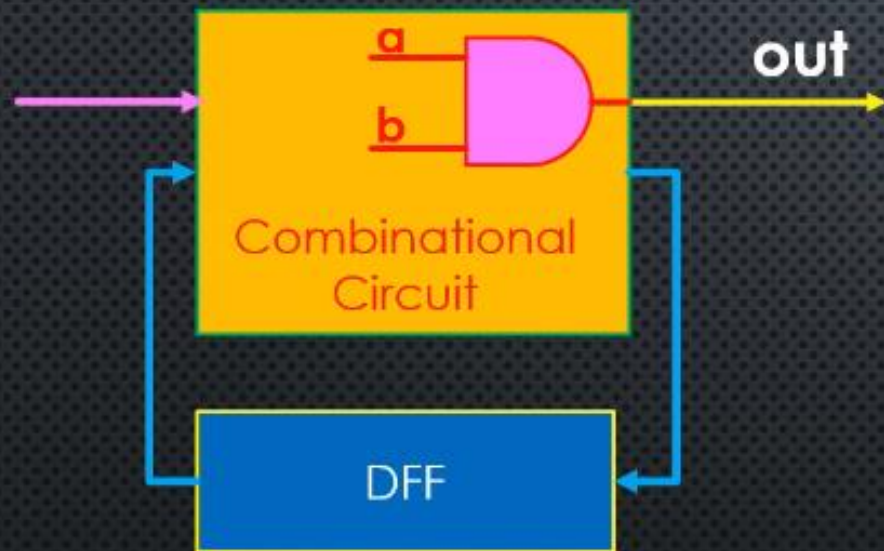

PARALLEL-SERIAL-PARALLEL LAB

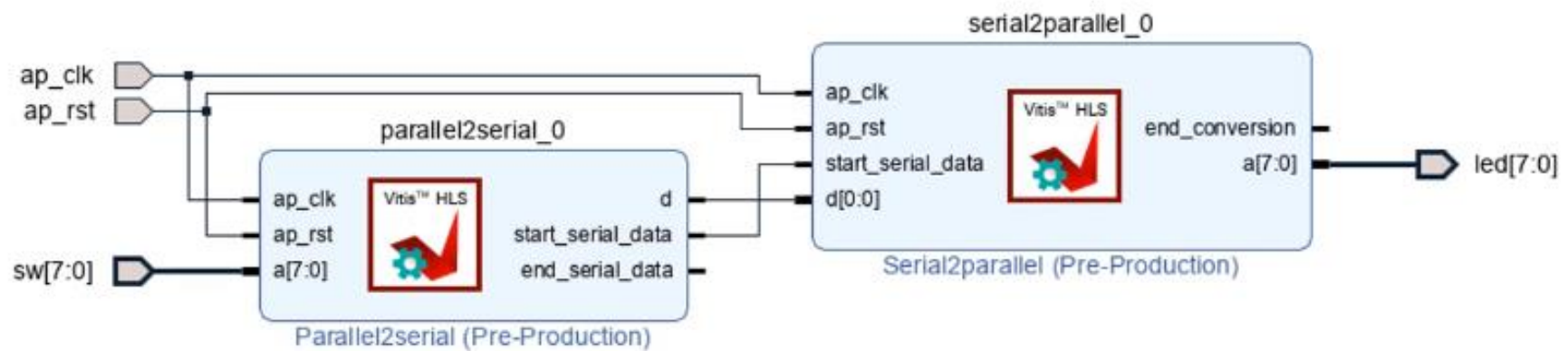 

HLS IMPLEMENTATION

Lecture 9

Any Question...

Thank you