 



DEBOUNCER

Lecture-10

SWITCH BOUNCING




SWITCH DEBOUNCING –SOLUTION

 

```
...  
currentBtnState = read_button(btnPin);  
if (currentBtnState != previousBtnState) {  
    lastDbncTime = millis();  
}  
  
if ((millis() - lastDbncTime) > dbnc_delay) {  
    currentLedState = currentBtnState;  
}  
....
```



SWITCH DEBOUNCING – HLS SOLUTION - IDEA

 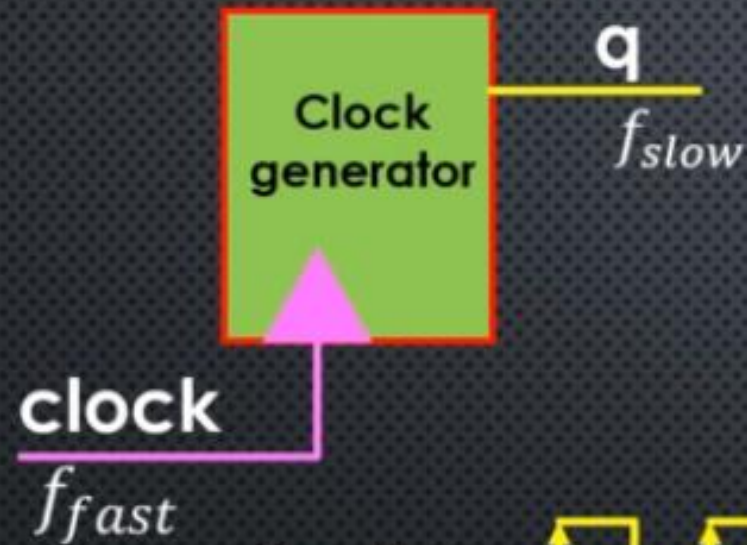

CLOCK GENERATOR


CLOCK DIVIDER

$$f_{slow} = \frac{1}{N} f_{fast}$$



$$f_{fast} = 100 \text{ MHz}$$
$$N = 1000$$
 
$$\longrightarrow f_{slow} = 100 \text{ KHz}$$



CLOCK DIVIDER

$$N = 20$$


$$f_{fast} = 100MHz$$



$$f_{slow} = 5MHz$$


$$T_{fast} = \frac{1}{100} = 10ns$$

$$T_{slow} = \frac{1}{5} = 200ns$$

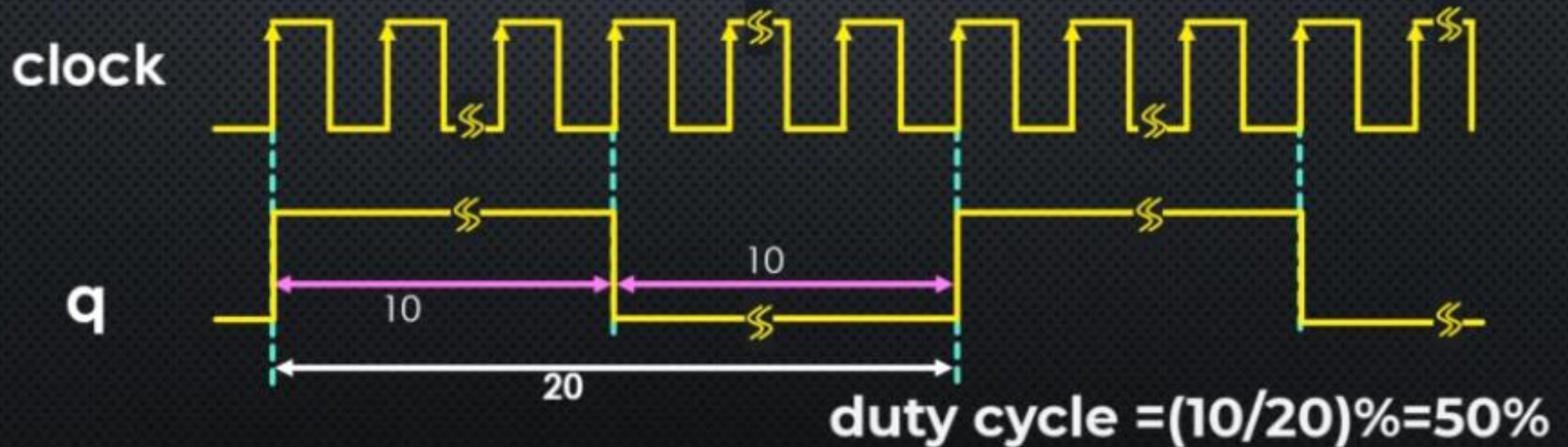


SINGLE-CYCLE PULSE GENERATOR

SINGLE CYCLE PULSE GENERATOR

 


PULSE GENERATOR - FSM

 



PULSE GENERATOR - FSM

Wait for 1
(W1)

Wait for 0
(W0)

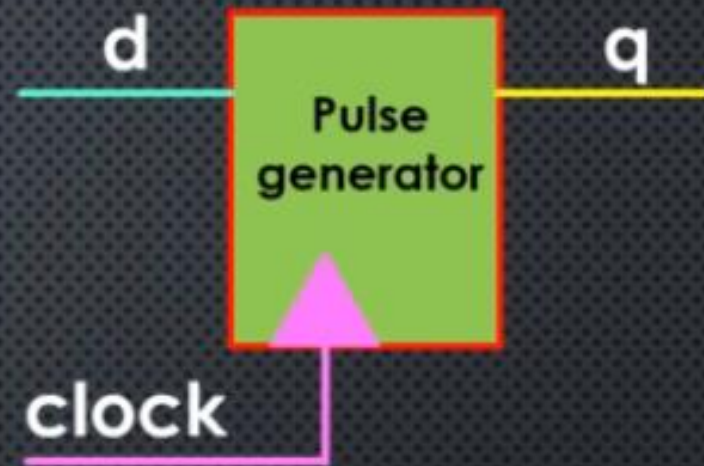

PULSE GENERATOR - FSM

 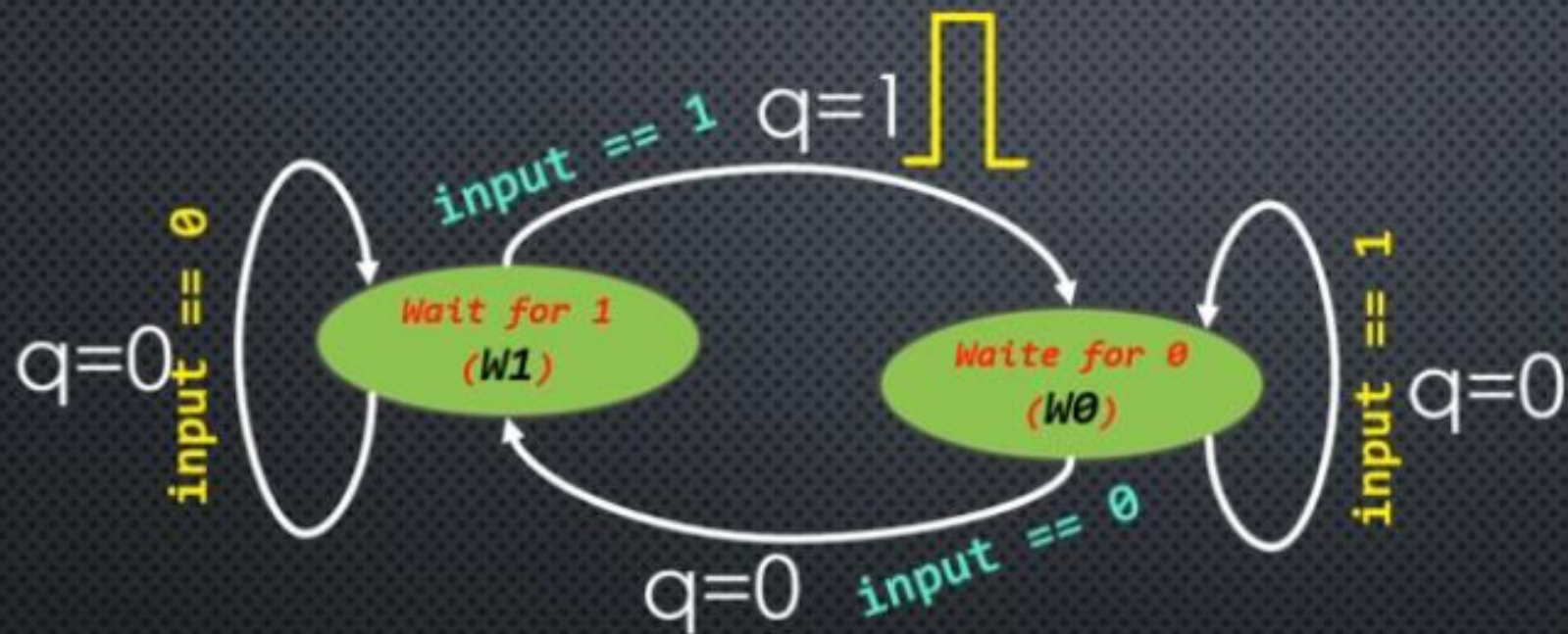

PULSE GENERATOR - HLS


```
typedef enum{W1, W0} pulse_gen_states_type;

void pulse_generator(bool input, bool &pulse) {
#pragma HLS INTERFACE ap_none port=input
#pragma HLS INTERFACE ap_none port=pulse
#pragma HLS INTERFACE ap_ctrl_none port=return

    static pulse_gen_states_type state = idle;

    pulse_gen_states_type next_state;
    bool next_pulse;

     switch(state) {
    case W1:
        ...
        break;
    case W0:
        ...
        break;
    default:
        break;
    }
    state = next_state;
    pulse = next_pulse;
}
```



PULSE GENERATOR - HLS

```
typedef enum{W1, W0} pulse_gen_states_type;
```

```
void pulse_generator(bool input, bool &pulse) {  
#pragma HLS INTERFACE ap_none port=input  
#pragma HLS INTERFACE ap_none port=pulse  
#pragma HLS INTERFACE ap_ctrl_none port=return
```


```
    static pulse_gen_states_type state = idle;
```

```
    pulse_gen_states_type next_state;  
    bool next_pulse;
```

```
    switch(state) {  
    case W1:  
        ...  
        break;  
    case W0:  
        ...  
        break;  
    default:  
        break;  
    }
```

```
    state = next_state;  
    pulse = next_pulse;
```

```
}
```

 



```
switch(state) {  
case W1:  
    if (input == 1) {  
        next_state = W0;  
        next_pulse = 1;  
    } else {  
        next_state = W1;  
        next_pulse = 0;  
    }  
    break;  
case W0:  
    if (input == 1) {  
        next_state = W0;  
        next_pulse = 0;  
    } else {  
        next_state = W1;  
        next_pulse = 0;  
    }  
    break;  
default:  
    break;  
}
```


ILA


OBJECTIVES

- ❖ Understanding the concept behind the ILA IP
- ❖ Customising the ILA IP
- ❖ Using the ILA IP to monitor signals in an HLS design


INTEGRATED LOGIC ANALYSER (ILA) IP

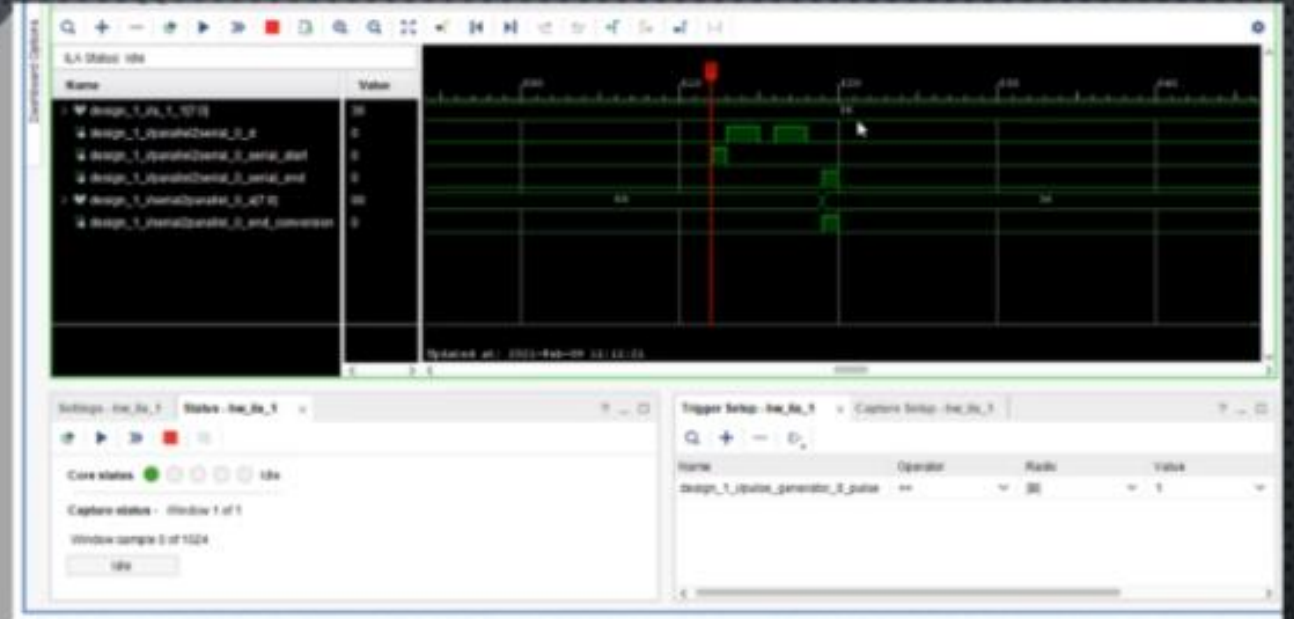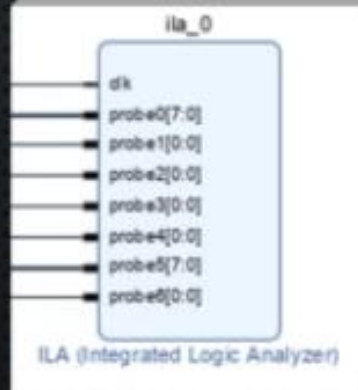


ILA IN A DESIGN

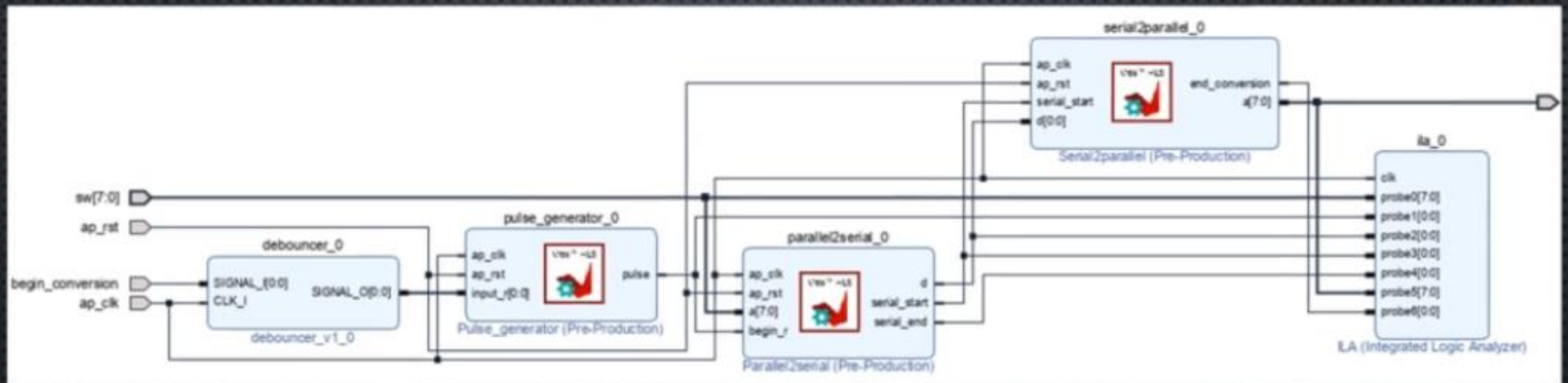

ILA CORE SYMBOL

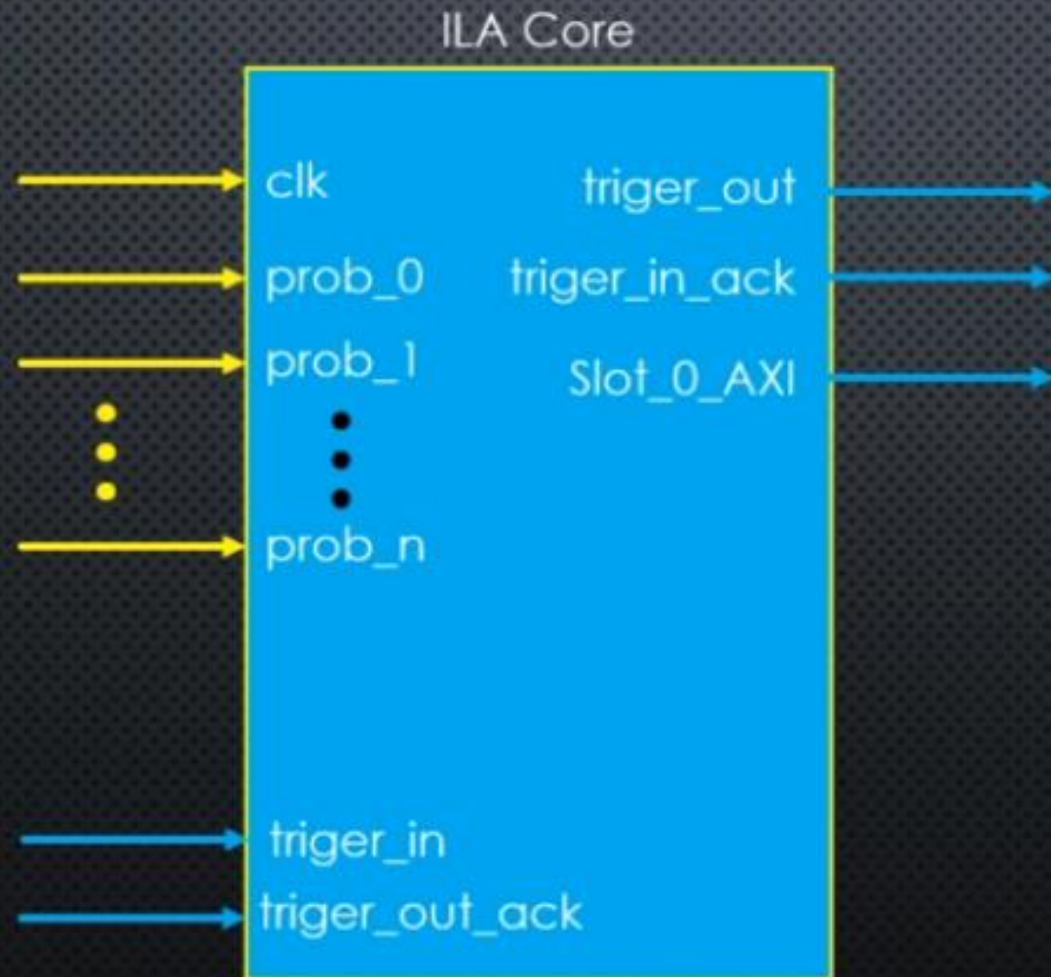

HOW DOES ILA WORK?

 

ILA DEBUG FLOW

Design Time

- ❖ Instantiation
- ❖ Customisation
- ❖ Connection


FPGA Programming

Runtime

- ❖ Define Trigger
- ❖ Run
- ❖ Inspection



ILA IN PARALLEL-TO-SERIAL-TO-PARALLEL

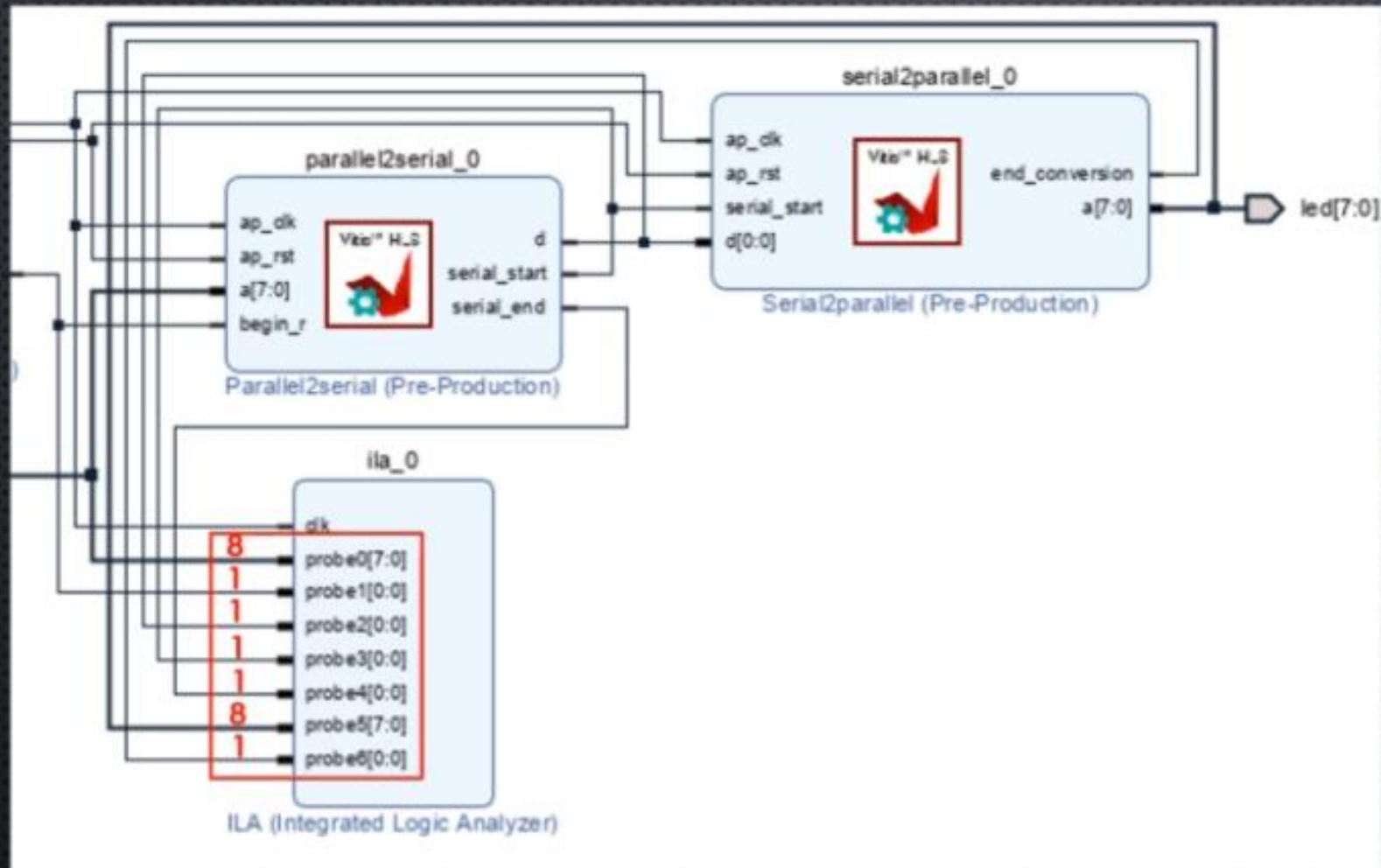

probe0	8	a (sw)
probe1	1	begin_r
probe2	1	d
probe3	1	serial_start
probe4	1	serial_end
probe5	8	a (led)
probe6	1	end_conversion

Any Question...

Thank you